

## EE-224 (Project)

### Little Computer Architecture

Sarvadnya Desai - 210040138

Ishaan Manhar - 210070033


Harsh Raj Chaudhari - 210040060

Akshat Teyaria - 210110014

### Specifications:

- ALU: Functions ADD, SUB, NAND, XOR along with Carry and Zero flags.
- Programmer Register (Register File): Contains 8 general purpose registers (R0 to R7) with R7 as PC (program counter)
- Multiple instantiations of Temporary Registers (T)
- Sign extender: A 16-bit extension to add leading zeros to numbers less than 16-bit.

## ALU DESIGN:

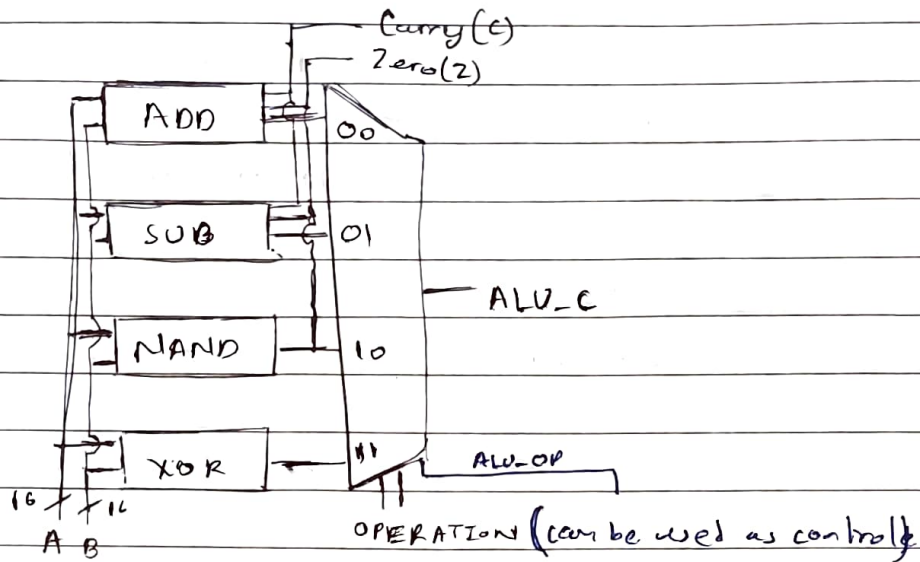


Input : ALU-A, ALU-B (16 bit)

Control: operation function code - (2 bit), ALU-op

Output: ALU-C and Carry and Zero Flags

(Operations Are functional.)

- Register File (8 registers):

 

INPUTS: IN (16-bit)


RF-D<sub>3</sub>, RF-A<sub>1</sub>, RF-A<sub>2</sub>, RF-A<sub>3</sub>  
~~RF-A<sub>0</sub>~~, ~~RF-A<sub>0</sub>~~  
 RF-B, RF-B

OUTPUTS:  $R_F, D, R_F, R$   
~~6~~ (16-bit)

CONTROL: WR<sub>2</sub>EN

We have 1 input demultiplexer and 2 output (read) multiplexers connected to the RF.

Temporary Register (T):

 

Sign Extension:

To be performed ~~via~~ bit shifting using behavioural modeling.  
Concatenate leading zeroes / (or 1s) as required.


ADD r<sub>c</sub>, r<sub>a</sub>, r<sub>b</sub>

S <sub>1</sub>	PC → Mem_Add	
	Mem_Data → T <sub>1</sub>	MRD
	PC → ALU_A	PCE
	+2 → ALU_B	ADD
	ALU_C → PC	T <sub>1</sub> :E

S <sub>2</sub>	T <sub>1</sub> (11-9) → RF_A <sub>1</sub>	
	T <sub>1</sub> (8-6) → RF_A <sub>2</sub>	T <sub>2</sub> :E
	RF_D <sub>1</sub> → T <sub>2</sub>	T <sub>3</sub> :E
	RF_D <sub>2</sub> → T <sub>3</sub>	

S <sub>3</sub>	T <sub>2</sub> → ALU_A	
	T <sub>3</sub> → ALU_B	ADD
	ALU_C → T <sub>2</sub>	T <sub>2</sub> :E


S <sub>4</sub>	T <sub>2</sub> → RF_D <sub>3</sub>	
	T <sub>1</sub> (5-3) → RF_A <sub>3</sub>	RFWE

 
 
## ADC and ADZ


ADC  $rc, ra, rb$

All the states are same as ADD, but there is one change in state diagram.



ADZ  $rc, ra, rb$

 Similarly states are same but change in state diagram.



## Clubbing the three state diagrams (ADD, ADC, ADZ)


C.Z  $\rightarrow$  2 bits that we have in instruction.

C-F, Z-F  $\rightarrow$  carry flag & zero flag generated in ALU & stored in a d-flip flop.

Truth Table when we perform Addition (go to  $S_2$  from  $S_1$ )

C	Z	C-F	Z-F
0	0	X	X
1	0	1	X
0	1	X	1
 
$$\text{condition} = \bar{C}\bar{Z} + C.C-F + Z.Z-F$$






AD1 rb,ra,imm6

All the states are the same except it ~~is~~  $S_2$ .

$S_5$	$T_1(11-q) \rightarrow RF\_A_1$ $T_1(5-0) \rightarrow SE6\_IN$ $SE6\_OUT \rightarrow T_2$ $RF\_D_3 \rightarrow T_3$	$T_2!E$ $T_3!E$
-------	--	--------------------

State diagram

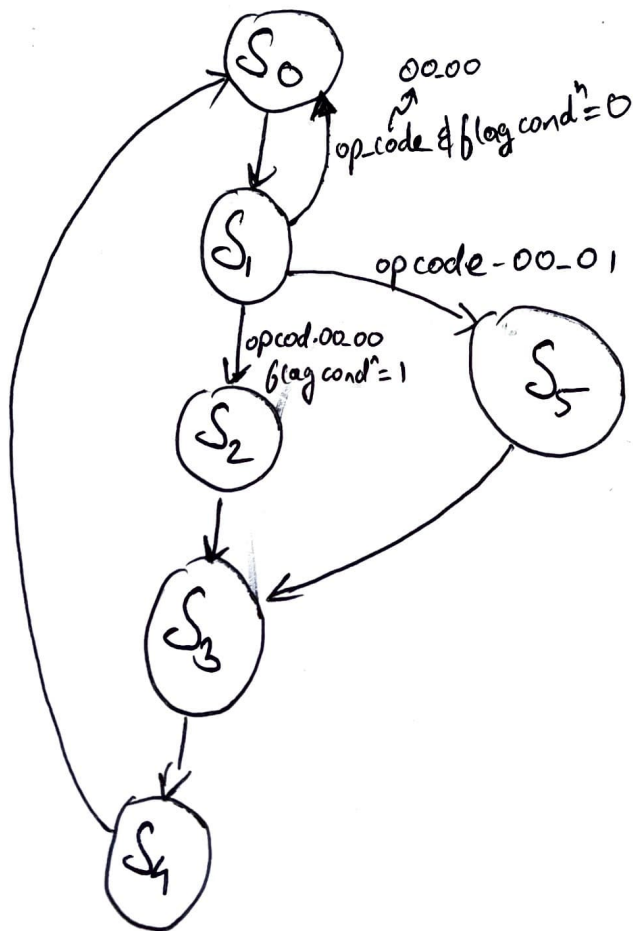

NDU / NDC / NDZ

①

S<sub>1</sub>:

PC → Mem_Add	T <sub>1</sub> WR
Mem_Add → T <sub>1</sub> (16-bits)	
PC → ALU_A	
+2 → ALU_B	ADD
ALU_C → PC	WR-EN

S<sub>2</sub>:

T <sub>1</sub> (11-9) → RF_A <sub>1</sub>	T <sub>2</sub> WR
T <sub>1</sub> (8-6) → RF_A <sub>2</sub>	T <sub>3</sub> WR
RF_D <sub>1</sub> → T <sub>2</sub>	
RF_D <sub>2</sub> → T <sub>3</sub>	

S<sub>3</sub>:

T <sub>2</sub> → ALU_A	
T <sub>3</sub> → ALU_B	
ALU_C → T <sub>2</sub>	NAND

S<sub>4</sub>:

T <sub>2</sub> → RF_A <sub>3</sub>
T <sub>1</sub> (5-3) → RF_D <sub>3</sub>

to incorporate NDZ and NDC we check condition:  
 $z \cdot z' + c \cdot c' + c' \cdot z' = 1$  before entering state 2.



✱

LW (LOAD):

15 12 11 9 8 6 5 0  
0100 RA RB Imm (6 bit)

① Read Instructions:

PC → Mem-add	
Mem-data → T1	T1-WR
PC → ALU-A	
+2 → ALU-B	ALU-OP
ALU-C → PC	WR-BN

② Understand / Read operands

T1 (8-6) → RF-A1	
RF-D1 → T2	T2-WR

③ Compute Address:

T2 → ALU-A	
Sign-Ext(T1 (5-0)) → ALU-B	ALU-OP
ALU-C → T2	T2-WR

④ Memory Reading:

T2 → Mem-Add	
Mem-Data → T2	T2-WR

⑤ Update:

T1 (11-9) → RF-A3	
T2 → RF-D3	WR-BN

✱

SW (STORE):

15 12 11 9 8 6 5 0  
0101 RA RB IMM

① Read Instruction:

PC → Mem-add	
Mem-data → T1	T1-WR
PC → ALU-A	
+2 → ALU-B	
ALU-C → PC	WR-BN

② Read Operands:

T1 (8-6) → RF-A1	
RF-D1 → T2	T2-WR
T2 (11-9) → RF-A2	
RF-D2 → T3	T3-WR

③ Compute Address:

T2 → ALU-A	
Sign-Ext(T1 (5-0)) → ALU-B	
ALU-C → T2	T2-WR

④ Transfer data to memory:

T2 → Mem-add	
T3 → Mem-data	MEM-WR

# LM (Load Multiple):

15	12	11	9	7	0
0110			RA	0	13 bits

① Read Instruction:

PC $\rightarrow$ Mem-add	
Mem-data $\rightarrow$ T1	T1-WR
PC $\rightarrow$ ALU-A	
+2 $\rightarrow$ ALU-B	ALU-OP
ALU-C $\rightarrow$ PC	WR-EN

② Store the next instruction, Read Operands:

PC $\rightarrow$ T2	T2-WR
T1(11-9) $\rightarrow$ RF-A1	
RF-D1 $\rightarrow$ T3	T3-WR

③ The Looping State:

④ SETTING UP FOR LOOPING:

T3 $\rightarrow$ MEM-ADD	
MEM-DATA $\rightarrow$ T4	T4-WR
T3 $\rightarrow$ ALU-A	
+2 $\rightarrow$ ALU-B	ALU-OP
ALU-C $\rightarrow$ T3	T3-WR
000 $\rightarrow$ T5(2-0)	T5-WR

⑤

T5(2-0) $\rightarrow$ RF-A3	
T4 $\rightarrow$ RF-D3	T1(0) $\rightarrow$ WR-EN
T5 $\rightarrow$ ALU-A	
+1 $\rightarrow$ ALU-B	ALU-OP
ALU-C $\rightarrow$ T5	T5-WR
T3 $\rightarrow$ MEM-ADD	
MEM-DATA $\rightarrow$ T4	T1(0) $\rightarrow$ T4-WR
T3 $\rightarrow$ ALU-A	
+2 $\rightarrow$ ALU-B	T1(1) $\rightarrow$ ALU-OP
ALU-C $\rightarrow$ T3	T1(0) $\rightarrow$ T3-WR

Repeat ⑤ for control T1(1), T1(2), ..., T1(6)

⑥ Writing k7:

T5(2-0) $\rightarrow$ RF-A3	T1(7) $\rightarrow$ WR-EN
<del>RF-D3</del> $\rightarrow$ RF-D3	

# STORE MULTIPLE (SM):

15	12	11	9	7	0
0101			RA	0	13 bits

① Read Instructions:

PC $\rightarrow$ Mem-Add	
Mem-data $\rightarrow$ T1	T1-WR
PC $\rightarrow$ ALU-A	
+2 $\rightarrow$ ALU-B	ALU-OP
ALU-C $\rightarrow$ PC	WR-EN

② Initiate counter, Read Operands:

000 $\rightarrow$ T2(2-0)	T2-WR
T1(11-9) $\rightarrow$ RF-A1	
RF-D1 $\rightarrow$ T3	T3-WR
T3 $\Rightarrow$	

③  
T4 = content

T3 → MEM_ADD	
MEM_DATA → T4	T4_WR
T3 → ALU_A	
+2 → ALU_B	T1(0) → ALU_OP
ALU_C → T3	T1(0) → T3_WR
T3(2-0) → RF_A3	
T4 → RF_D3	T1(0) → RF_EN
T2 → ALU_A	
+1 → ALU_B	
ALU_C → T2	T2_WR

③ Control Loop!

T2(2-0) → RF_A1	
RF_D1 → T4	T1(0) → T4_WR
T3 → MEM_ADD	
T4_WR → MEM_DATA	T1(0) → MEM_WR
T3 → ALU_A	
+2 → ALU_B	T1(0) → ALU_OP
ALU_C → T3	T1(0) → T3_WR
T2 → ALU_A	
+1 → ALU_B	ALU_OP
ALU_C → T2	T2_WR

- Repeat step ③ for T1(0), T1(1), T1(2), ..., T1(7).



IHI: 00-11 RA Imm  
15-12 11-9 8-0

S <sub>1</sub> :	PC → Mem. Add Mem. Data → T1 PC → ALU-A +2 → ALU-B ALU.C → PC	T1.WR  ADD WR.EN
------------------	---	---------------------------

S <sub>2</sub> :	T <sub>11(8→0)</sub> → [75] [75] → RF-D <sub>3</sub> T <sub>11(11→9)</sub> → RF-A <sub>3</sub>	WR.EN
------------------	--	-------

→ Shifts the 9 bits Imm by 7 bits  
↓  
Multiplying by 100000000

REQ: 11-00 RA RB Imm  
15-12 11-9 8-6 5-0

S <sub>1</sub> :	PC → Mem. Add Mem. Data → T1 PC → ALU-A +2 → ALU-B ALU.C → PC	T1.WR  ADD WR.EN
------------------	---	---------------------------

S <sub>2</sub> :	T <sub>11(11→9)</sub> → RF-A <sub>1</sub> T <sub>11(8→6)</sub> → RF-A <sub>2</sub> RF-D <sub>1</sub> → T <sub>2</sub> RF-D <sub>2</sub> → T <sub>3</sub> T <sub>11(5-0)</sub> <u>SE16</u> → ALU-A T <sub>2</sub> → ALU-B ALU.C → T <sub>4</sub>	T2.WR T3.WR  SUB T4.WR
------------------	---	------------------------------------

→ Storing value from RA and RB in T2 and T4  
and computing Imm-2

S <sub>3</sub> :	T <sub>2</sub> → ALU-A T <sub>3</sub> → ALU-B ALU-Z → Z	SUB Z.WR
------------------	---	-------------

→ checking Cond<sup>n</sup>

S <sub>4</sub> :	T <sub>4</sub> → ALU-A If (Z=1) then T <sub>11(5→0)</sub> → ALU-B Flag 0 → ALU.B ALU.C → PC	ADD
------------------	---	-----



JAL: 10 00 RA RA Imm  
15 12 11 9 8 0

S1:	PC $\rightarrow$ Mem_Add	TI-WR
	Mem_Data $\rightarrow$ T1	
	PC $\rightarrow$ T2	
	PC $\rightarrow$ ALU-A	ADD
	T2 $\rightarrow$ ALU-B	
	ALU-C $\rightarrow$ PC	WR-EN

S2:	T2 $\rightarrow$ RF-D3	WR-EN
	T1(11-0) $\rightarrow$ RF-A3	
	T1(8-0) $\xrightarrow{SE16}$ ALU-A	SUB
	2 $\rightarrow$ ALU-B	
	ALU-C $\rightarrow$ T2	T2-WR

- ① Storing PC in RA  
② Computing Imm-2 and Storing in T2

S3:	T2 $\rightarrow$ ALU-A	
	PC $\rightarrow$ ALU-B	WR-EN
	ALU-C $\rightarrow$ PC	

## JALR

10 01 RA RB Imm  
(15-12) (11-9) (8-6)

S1: Same as JAL

S2:	T2 $\rightarrow$ RF-D3	WR-EN
	T1(11-0) $\rightarrow$ RF-A3	
	T1(8-0) $\rightarrow$ RF-A1	
	RF-D1 $\rightarrow$ T2	T2-WR

- ① Storing PC in RA  
② Storing Address in RB to T2

S3:	T2 $\rightarrow$ PC	T2-WR
-----	---------------------	-------

# STATE DIAGRAM FOR THE CPU:

